
PROJECT ON VLSI

Design, layout of logic gates
using electric tool and LT-Spice

First standard cell : 2-input NOR gate Schematic-

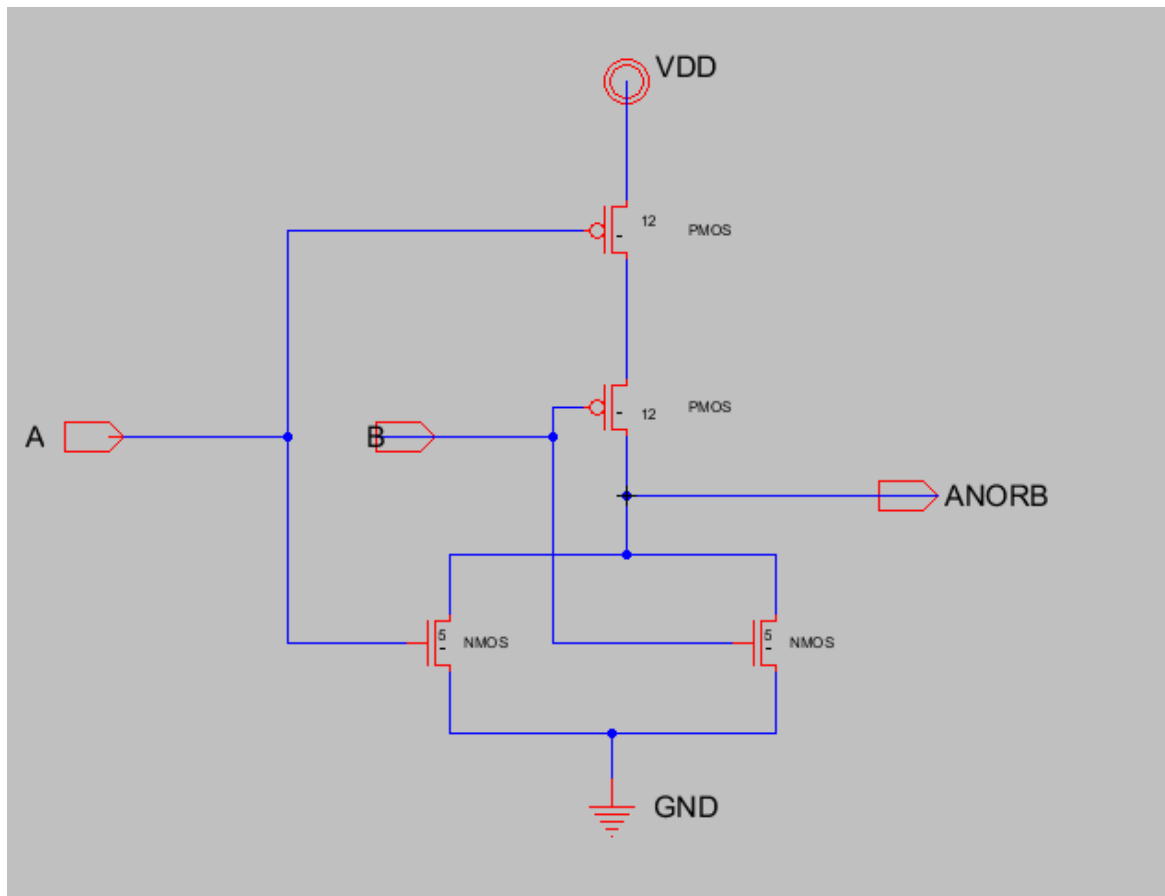


Fig 1: NOR Schematic

NOR gate sizing- For choosing the sizes, I have applied following signal and measured its rise and fall time.

VIN1 A 0 PULSE 0 'SUPPLY' 100PS 20PS 20PS 500PS 1000PS

VIN2 B 0 PULSE 0 'SUPPLY' 200PS 20PS 20PS 500PS 1000PS

And changed the sizes of p-MOS and n-MOS such that its rise and fall time becomes equal. The sizes of the n-MOS and p-MOS, for which rise and fall time are equal, I have chosen that size.

n-MOS=5

p-MOS=12

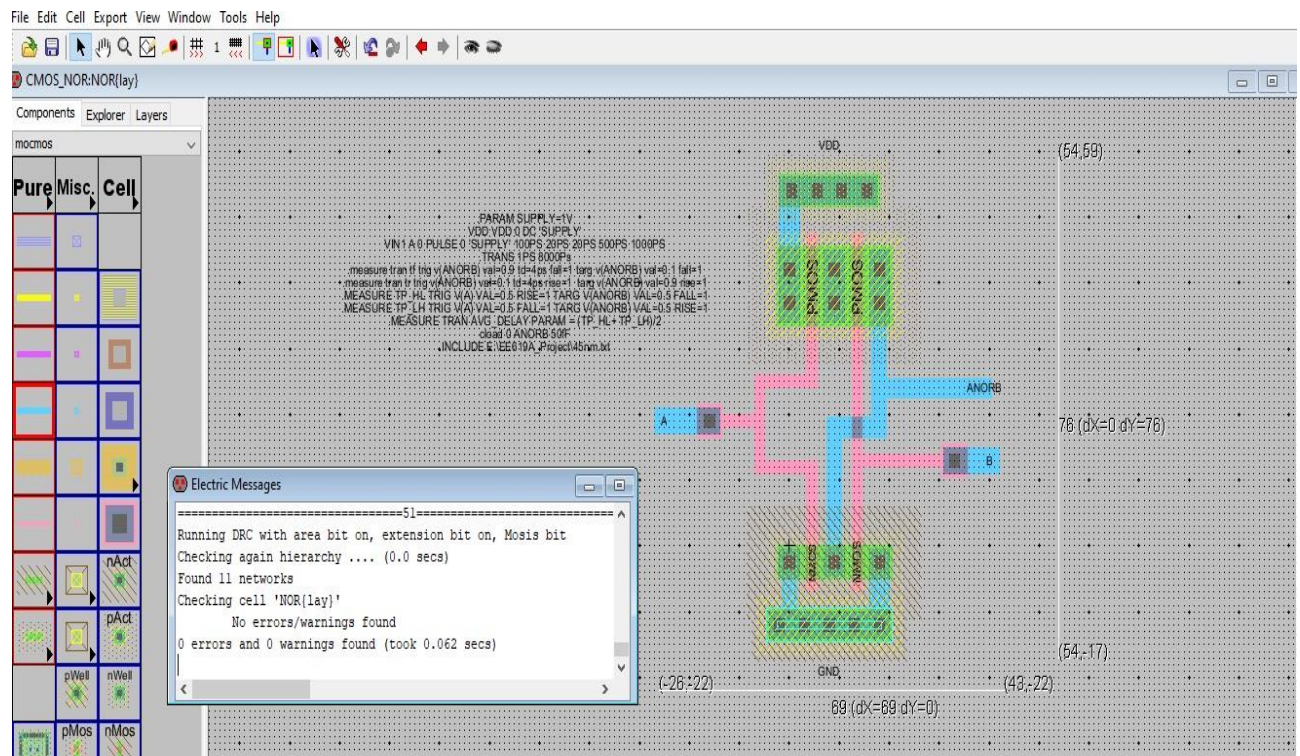


Fig2: NOR LAYOUT WITH DRC LOG

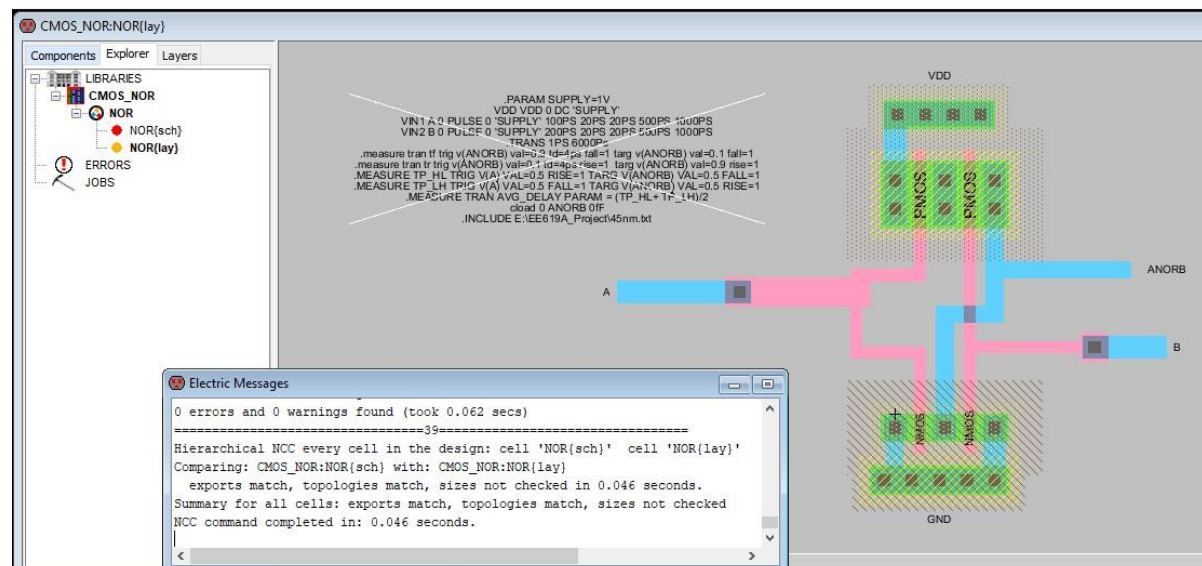


Fig3: NOR LAYOUT WITH LVS LOG

Propagation delay-

Table – 1. Propagation delays from schematic

Load (C_L)	t_{phl}	t_{plh}	t_p
5 fF	2.77×10^{-11}	3.26×10^{-11}	3.018×10^{-11}
50 fF	1.99×10^{-10}	2.44×10^{-10}	2.219×10^{-10}

Table – 2. Propagation delays from layout

Load (C_L)	t_{phl}	t_{plh}	t_p
5 fF	3.033×10^{-11}	3.593×10^{-11}	3.313×10^{-11}
50 fF	2.025×10^{-10}	2.472×10^{-10}	2.249×10^{-10}

Power consumption

Table – 3. Power Consumption

	$C_L = 5 \text{ fF}$	$C_L = 50 \text{ fF}$
Schematic	-5.816uW	-41.72 uW
Layout	-6.5241 uW	-41.953 uW

Waveforms-

Input values used for generating waveforms-

VIN1 A 0 PULSE 0 'SUPPLY' 200PS 20PS 20PS 900PS 2000PS

VIN2 B 0 PULSE 0 'SUPPLY' 2200PS 20PS 20PS 900PS 2000PS

.TRANS 1PS 8000Ps

 


Fig 4: Waveform from schematic of input and output for 5fF

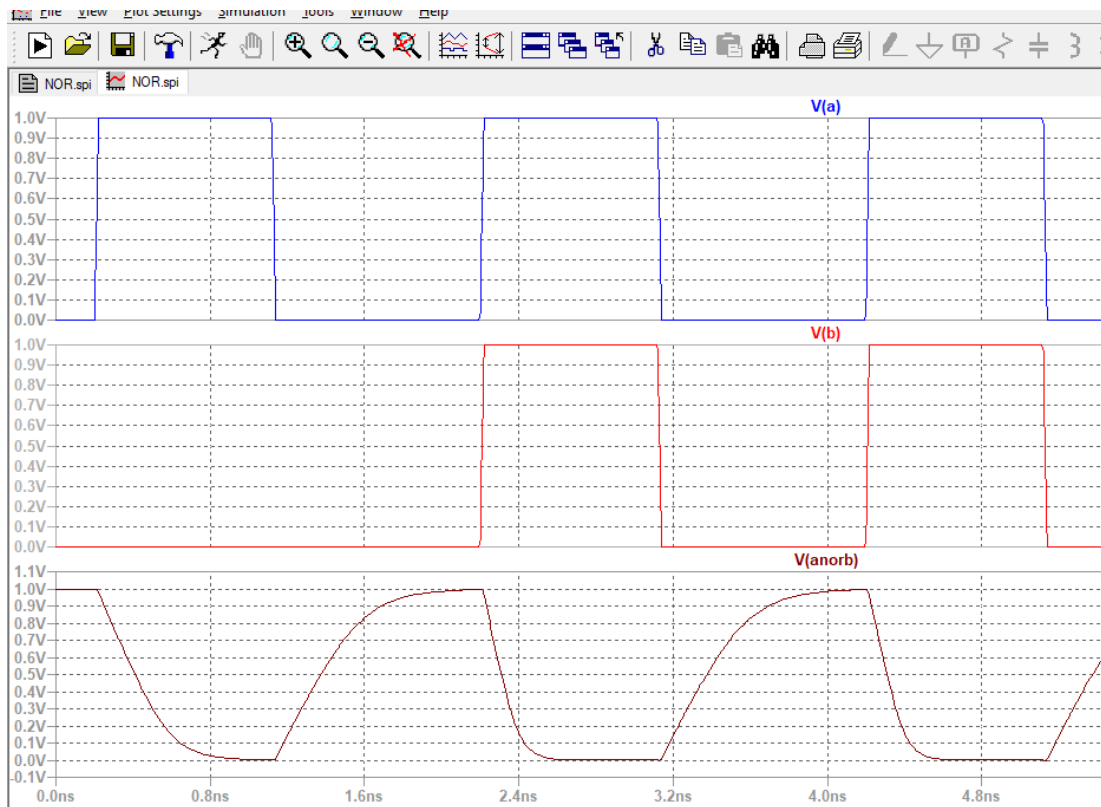


Fig 5: Waveform from schematic of input and output for 5fF

 


Fig 6: Waveform from Layout of input and output for 5fF

 


Fig 7: Waveform from Layout of input and output for 5fF

Second standard cell : 2-input NAND gate

Schematic-

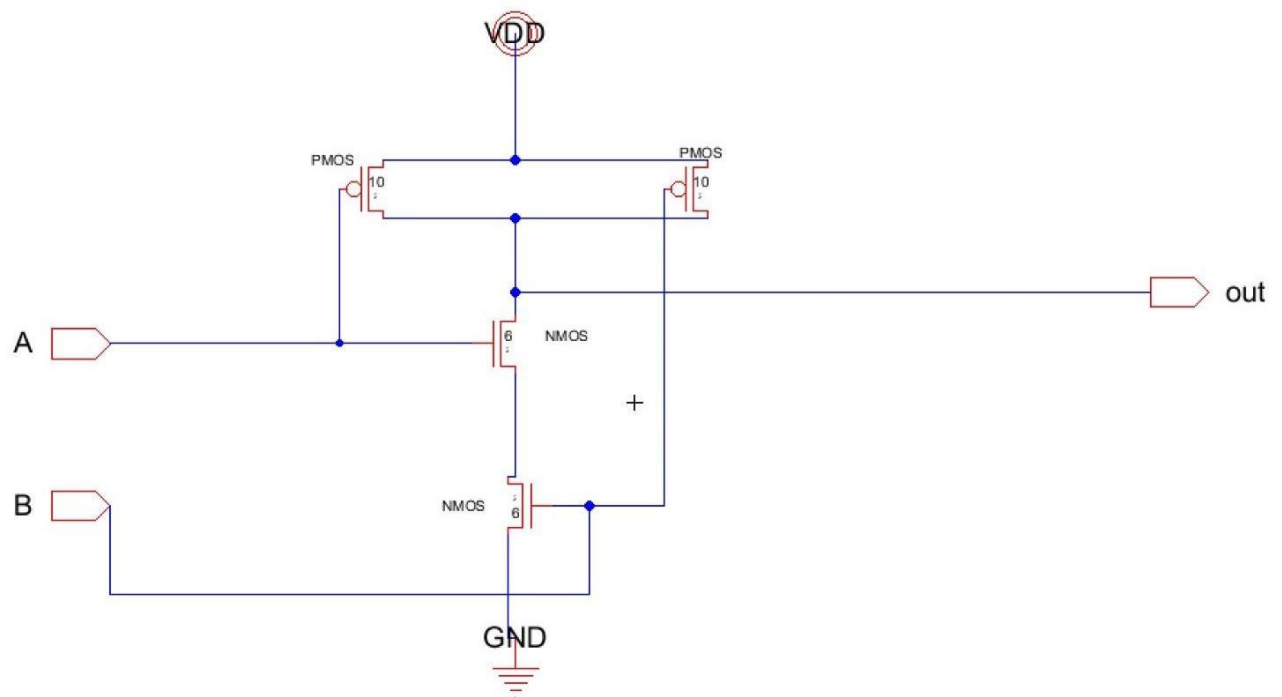


Fig – 1. NAND Schematic

NAND gate sizing- For choosing the sizes, I have applied following signal and measured its rise and fall time.

VIN1 A 0 PULSE 0 'SUPPLY' 100PS 20PS 20PS 300PS 500PS

VIN2 B 0 PULSE 0 'SUPPLY' 640PS 20PS 20PS 200PS 500PS

And changed the sizes of p-MOS and n-MOS such that its rise and fall time becomes equal. The sizes of the n-MOS and p-MOS, for which rise and fall time are equal, I have chosen that size.

n-MOS=6

p-MOS=10

Layout with the DRC log

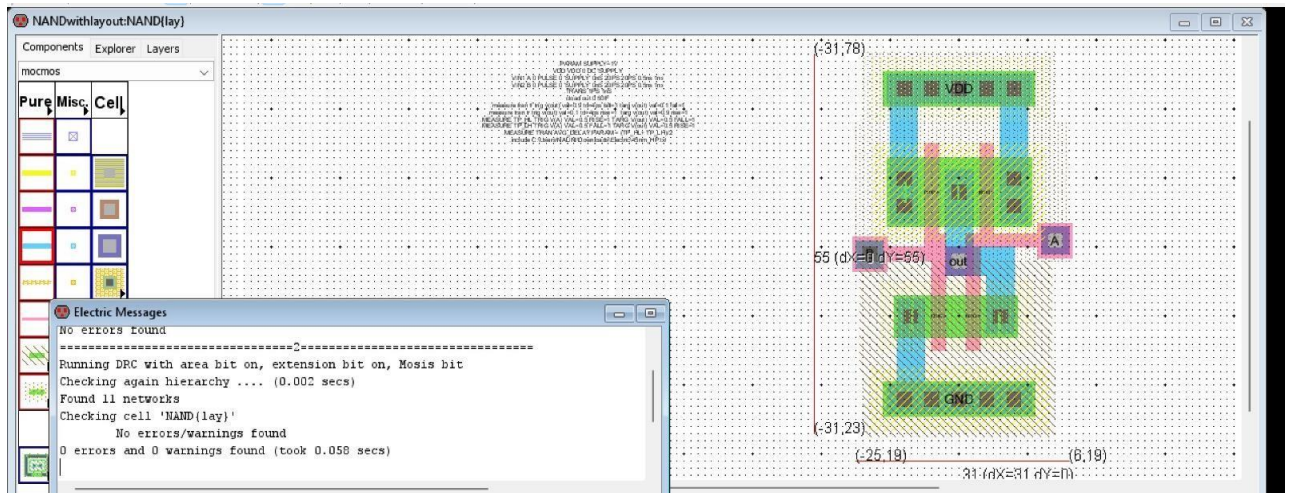


Fig – 2. NAND with DRC log

Layout with the LVS log

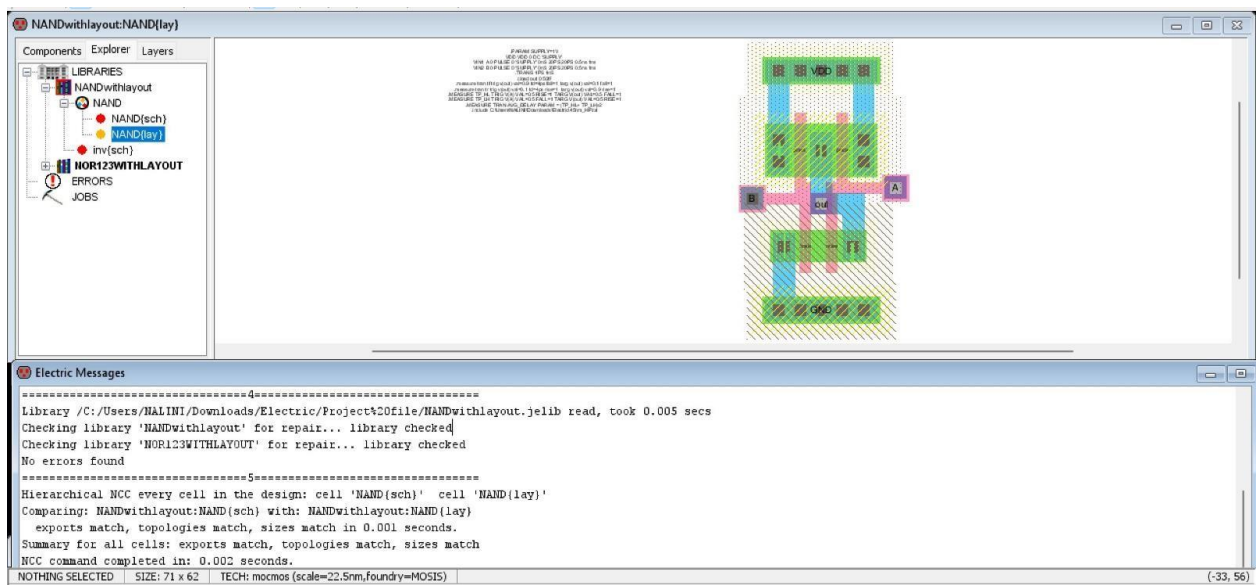


Fig – 3. NAND with LVS log

Propagation delay-

Table – 1. Propagation delays from schematic

Load (C_L)	t_{phl}	t_{plh}	t_p
5 fF	3.39×10^{-11}	1.24×10^{-11}	2.31×10^{-11}
50 fF	2.94×10^{-10}	6.18×10^{-11}	17.79×10^{-11}

Table – 2. Propagation delays from layout

Load (C_L)	t_{phl}	t_{plh}	t_p
5 fF	4.01×10^{-11}	1.26×10^{-11}	2.63×10^{-11}
50 fF	5.92×10^{-10}	1.55×10^{-10}	3.73×10^{-10}

Power consumption

Table – 3. Power Consumption

	$C_L = 5 \text{ fF}$	$C_L = 50 \text{ fF}$
Schematic	-5.88 μW	-40.73 μW
Layout	-6.03 μW	-40.82 μW

Waveforms-

Input values used for generating waveforms-

VIN1 A 0 PULSE 0 'SUPPLY' 100PS 20PS 20PS 300PS 500PS

VIN2 B 0 PULSE 0 'SUPPLY' 640PS 20PS 20PS 200PS 500PS

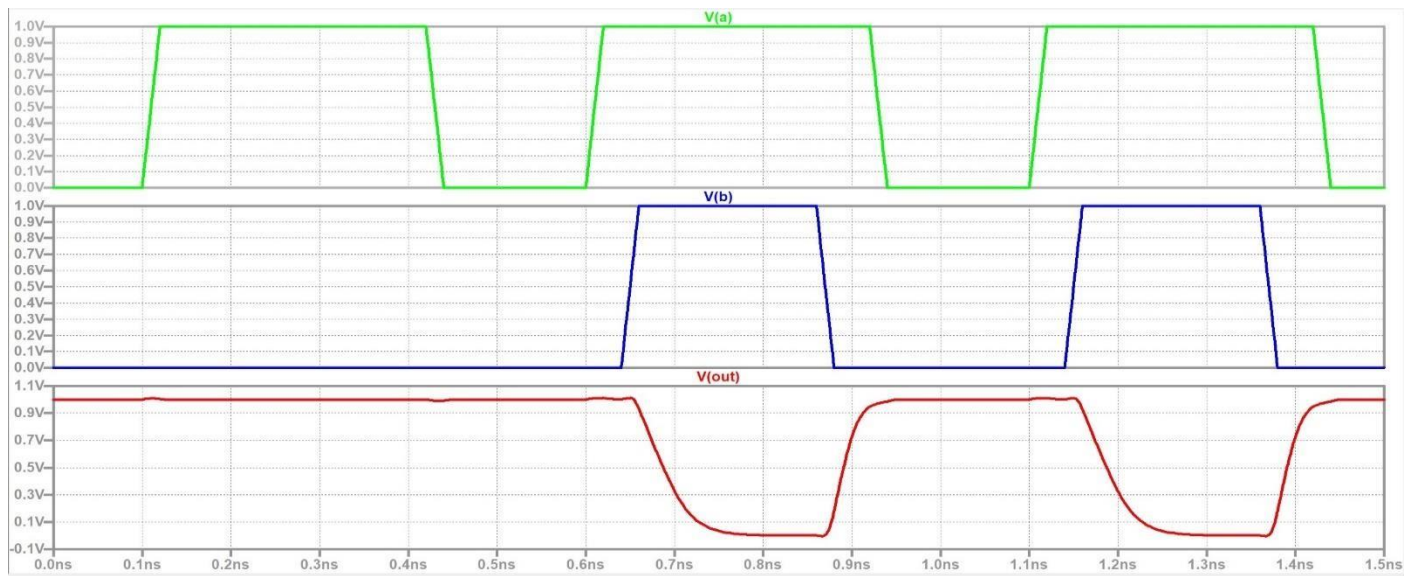


Fig – 4. Waveform from schematic with $C_L = 5$ fF

 


Fig – 5. Waveform from layout with $C_L = 5$ fF

 


Fig – 6. Waveform from schematic with $C_L = 50$ fF

 


Fig – 7. Waveform from layout with $C_L = 50$ fF